EE446 - LAB 5

PRELIMINARY WORK


Table of Contents

1.	Con	itrolle	er Design	2
	1.1.	ISA		2
	1.1.	1.	Data Processing	2
	1.1.	2.	Branch	4
	1.1.	3.	LDR / STR	4
	1.2.	Conf	troller Unit Design	5
	1.2.	1.	FSM	5
2.	Vali	datio	n	7
	2.1.	Ever	n – Odd	7
	2.2.	2's C	Compliment	8
			y Addition	

1. Controller Design

1.1. ISA

1.1.1. Data Processing

 


1.1.1.1. ALU Function

Assembler Mnemonic	OpCode	Action
AND	0000	operand1 AND operand2
EOR	0001	operand1 EOR operand2
SUB	0010	operand1 - operand2
RSB	0011	operand2 - operand1
ADD	0100	operand1 + operand2
ADC	0101	operand1 + operand2 + carry
SBC	0110	operand1 - operand2 + carry - 1
RSC	0111	operand2 - operand1 + carry - 1
TST	1000	as AND, but result is not written
TEQ	1001	as EOR, but result is not written
CMP	1010	as SUB, but result is not written
CMN	1011	as ADD, but result is not written
ORR	1100	operand1 OR operand2
MOV	1101	operand2(operand1 is ignored)
BIC	1110	operand1 AND NOT operand2(Bit clear)
MVN	1111	NOT operand2(operand1 is ignored)


AND, ORR, EOR, BIC, ADD, SUB, CMP, MOV are implemented

1.1.1.2. Shifter

 

Immediate shifter and register shifter is implemented. (LSL, LSR, ASR, ROR, ROL)

1.1.2. Branch

 


B and BL is implemented.

BX is implemented as:


BX Rn -> MOV R15, Rn

1.1.3. LDR / STR

 

1.2. Controller Unit Design

1.2.1. FSM

 


From	То	Condition
S0_Fetch	S1_Decode	
S1_Decode	S10_BranchLink	(Func[4]).(Decoder0)
S1_Decode	S7_Executel	(Func[5]).(Decoder0)
S1_Decode	S2_MemAdr	(Decoder0)
S1_Decode	S0_Fetch	(Decoder0)
S1_Decode	S6_ExecuteR	(!Func[5]).(Decoder0)
S1_Decode	S9_Branch	(!Func[4]).(Decoder0)
S2_MemAdr	S3_MemRead	(Func[0])
S2_MemAdr	S5_MemWrite	(!Func[0])
S3_MemRead	S4_MemWB	
S4_MemWB	S0_Fetch	
S5_MemWrite	S0_Fetch	
S6_ExecuteR	S8_ALUWB	
S7_ExecuteI	S8_ALUWB	
S8_ALUWB	S0_Fetch	
S9_Branch	S0_Fetch	
S10_BranchLink	S0_Fetch	

Control Signals

PCWrite
RegWrite
MemWrite
IRWrite
AdrSrc
ResultSrc
ALUSrcA
ALUSrcB
ImmSrc
RegSrc
ALUControl
BL_Active
Shifter_En
State


FSM Circuitry

 


2. Validation

2.1. Even – Odd


Even:

 

Odd:

 

2.2. 2's Compliment

 

2.3. Array Addition

Array: [5, 4, 3, 2, 1]

